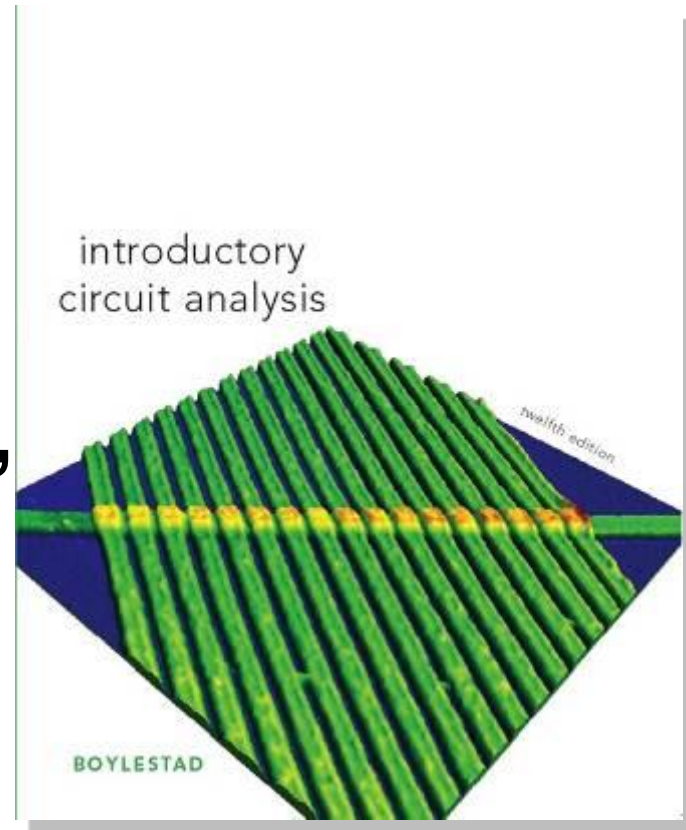


Chapter 14

The Basic Elements and Phasors, power, impedance



OBJECTIVES

- Become familiar with the response of a resistor, an inductor, and a capacitor to the application of a sinusoidal voltage or current.
- Learn impedance
- Understand how to calculate power B

DERIVATIVE

- To understand the response of the basic R , L , and C elements to a sinusoidal signal, you need to examine the concept of the **derivative** in some detail.

RESPONSE OF BASIC R, L, AND C ELEMENTS TO A SINUSOIDAL VOLTAGE OR CURRENT

- Resistor
- Inductor
- Capacitor

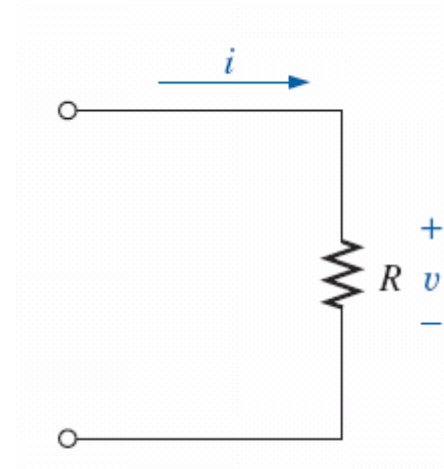


FIG. 14.4 *Determining the sinusoidal response for a resistive element.*

RESPONSE OF BASIC R, L, AND C ELEMENTS TO A SINUSOIDAL VOLTAGE OR CURRENT

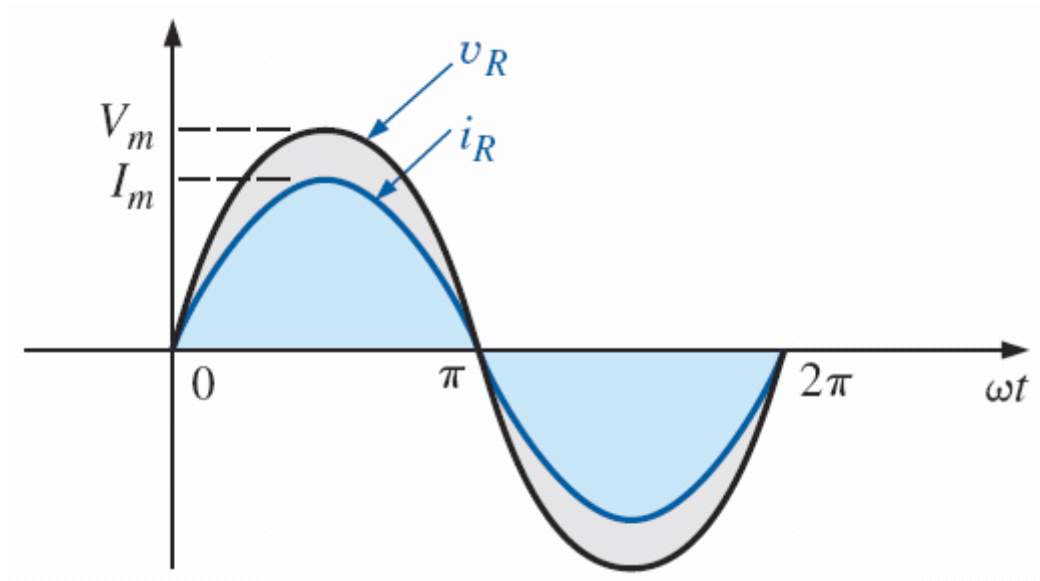


FIG. 14.5 The voltage and current of a resistive element are in phase.

RESPONSE OF BASIC R, L, AND C ELEMENTS TO A SINUSOIDAL VOLTAGE OR CURRENT

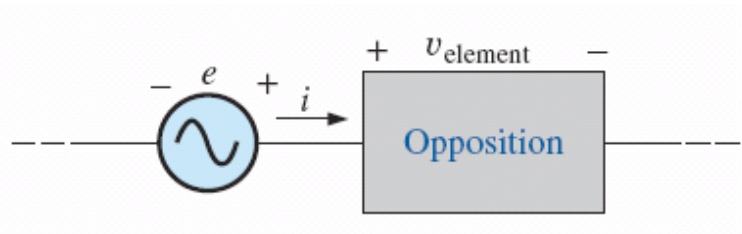


FIG. 14.6 Defining the opposition of an element to the flow of charge through the element.

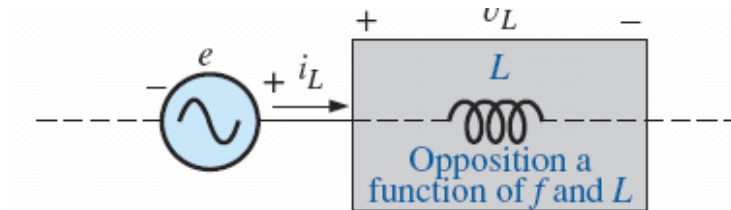


FIG. 14.7 Defining the parameters that determine the opposition of an inductive element to the flow of charge.

RESPONSE OF BASIC R, L, AND C ELEMENTS TO A SINUSOIDAL VOLTAGE OR CURRENT

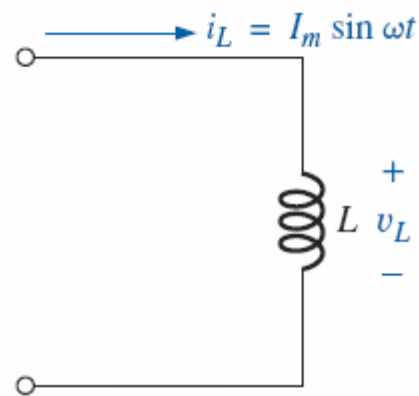


FIG. 14.8 Investigating the sinusoidal response of an inductive element.

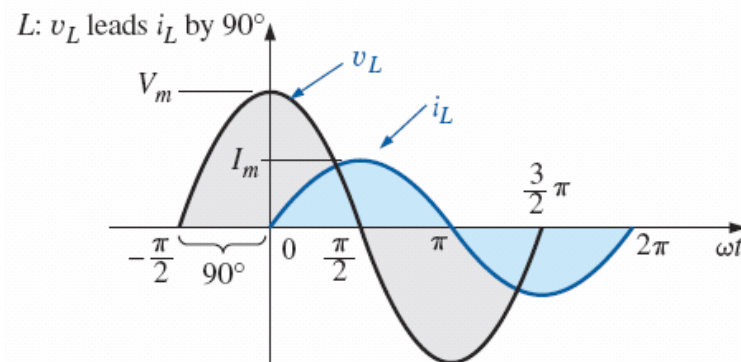


FIG. 14.9 For a pure inductor, the voltage across the coil leads the current through the coil by 90° .

RESPONSE OF BASIC R, L, AND C ELEMENTS TO A SINUSOIDAL VOLTAGE OR CURRENT

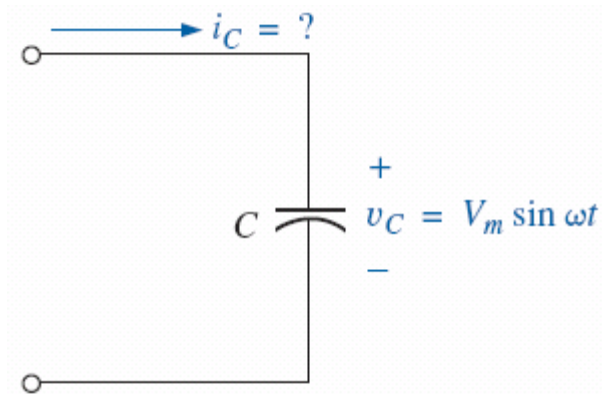


FIG. 14.11 Investigating the sinusoidal response of a capacitive element.

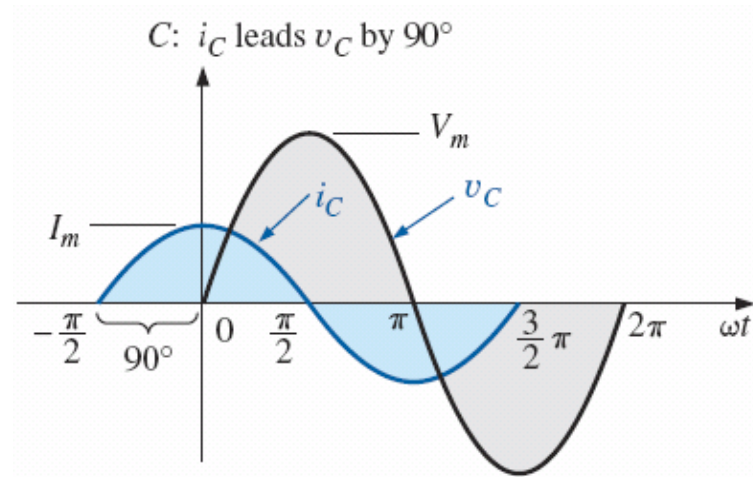


FIG. 14.12 The current of a purely capacitive element leads the voltage across the element by 90° .